

Choose and write the correct option(s) in the following questions.

1. Consider a current carrying wire (current  $I$ ) in the shape of a circle. Note that as the current progresses along the wire, the direction of  $j$  (current density) changes in an exact manner, while the current  $I$  remain unaffected. The agent that is essentially responsible for is


[NCERT Exemplar]

- (a) source of emf.
- (b) electric field produced by charges accumulated on the surface of wire.
- (c) the charges just behind a given segment of wire which push them just the right way by repulsion.
- (d) the charges ahead.

2. Two batteries of emf  $\epsilon_1$  and  $\epsilon_2$  ( $\epsilon_2 > \epsilon_1$ ) and internal resistances  $r_1$  and  $r_2$  respectively are connected in parallel as shown in Figure.

[NCERT Exemplar]

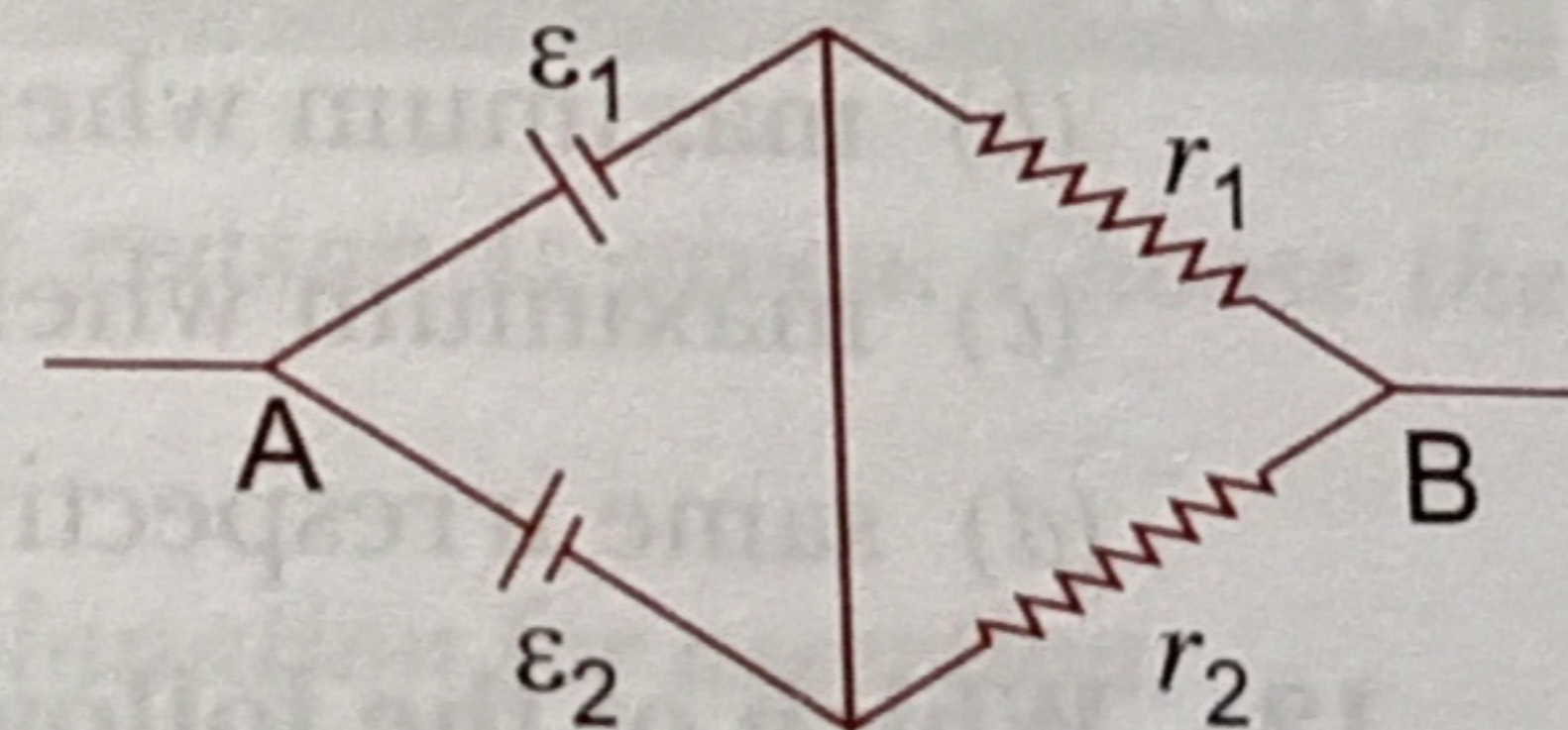- (a) The equivalent emf  $\epsilon_{eq}$  of the two cells is between  $\epsilon_1$  and  $\epsilon_2$ ,  
i.e.  $\epsilon_1 < \epsilon_{eq} < \epsilon_2$
- (b) The equivalent emf  $\epsilon_{eq}$  is smaller than  $\epsilon_1$ .
- (c) The  $\epsilon_{eq}$  is given by  $\epsilon_{eq} = \epsilon_1 + \epsilon_2$  always.
- (d)  $\epsilon_{eq}$  is independent of internal resistances  $r_1$  and  $r_2$ .



3. The drift velocity of the free electrons in a conducting wire carrying a current  $i$  is  $v$ . If in a wire of the same metal, but of double the radius, the current be  $2i$ , then the drift velocity of the electrons will be

- (a)  $v/4$
- (b)  $v/2$
- (c)  $v$
- (d)  $4v$

4. Assume that each atom of copper contributes one free electron. If the current flowing through a copper wire of 1 mm diameter is 1.1 A, the drift velocity of electrons will be

- (Density of Cu =  $9 \times 10^3 \text{ kg/m}^3$ , At. wt. of Cu = 63, Avogadro number =  $6.02 \times 10^{26}/\text{kg atom}$ )
- (a) 0.3 mm/s
  - (b) 0.5 mm/s
  - (c) 0.1 mm/s
  - (d) 0.2 mm/s

5. A resistance  $R$  is to be measured using a meter bridge. Student chooses the standard resistance  $S$  to be  $100\Omega$ . He finds the null point at  $l_1 = 2.9$  cm. He is told to attempt to improve the accuracy. Which of the following is a useful way? [NCERT Exemplar]

- (a) He should measure  $l_1$  more accurately.
- (b) He should change  $S$  to  $1000\Omega$  and repeat the experiment.
- (c) He should change  $S$  to  $3\Omega$  and repeat the experiment.
- (d) He should give up hope of a more accurate measurement with a meter bridge.

6. Two cells of emf's approximately  $5V$  and  $10V$  are to be accurately compared using a potentiometer of length  $400$  cm. [NCERT Exemplar]

- (a) The battery that runs the potentiometer should have voltage of  $8V$ .
- (b) The battery of potentiometer can have a voltage of  $15V$  and  $R$  adjusted so that the potential drop across the wire slightly exceeds  $10V$ .
- (c) The first portion of  $50$  cm of wire itself should have a potential drop of  $10V$ .
- (d) Potentiometer is usually used for comparing resistances and not voltages.


7. If a copper wire is stretched to make it  $0.1\%$  longer, the percentage increase in resistance will be

- (a)  $0.2$
- (b)  $2$
- (c)  $1$
- (d)  $0.1$

8. The resistivity of iron is  $1 \times 10^{-7}$  ohm-meter. The resistance of the given wire of a particular thickness and length is  $1$  ohm. If the diameter and length of the wire both are doubled the resistivity will be (in ohm-meter)

- (a)  $1 \times 10^{-7}$
- (b)  $2 \times 10^{-7}$
- (c)  $4 \times 10^{-7}$
- (d)  $8 \times 10^{-7}$

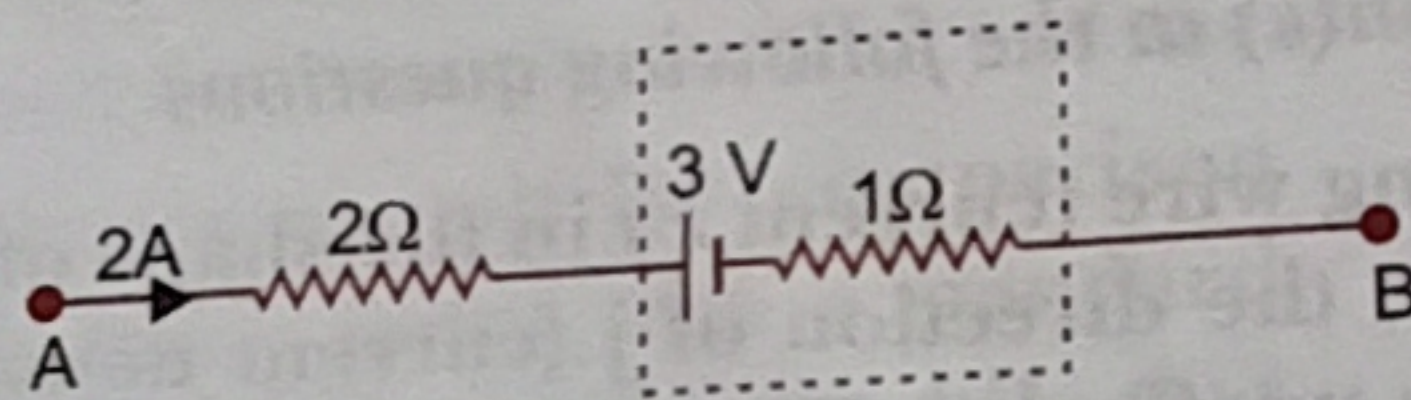9. Figure represents a part of a closed circuit. The potential difference between points  $A$  and  $B$  ( $V_A - V_B$ ) is



- (a)  $+9V$
- (b)  $-9V$
- (c)  $+3V$
- (d)  $+6V$

10. A student connects  $10$  dry cells each of emf  $E$  and internal resistance  $r$  in series, but by mistake the one cell gets wrongly connected. Then net emf and net internal resistance of the combination will be

- (a)  $8E, 8r$
- (b)  $8E, 10r$
- (c)  $10E, 10r$
- (d)  $8E, \frac{r}{10}$

11. A metal rod of length  $10$  cm and a rectangular cross-section of  $1\text{cm} \times \frac{1}{2}\text{cm}$  is connected to a battery across opposite faces. The resistance will be [NCERT Exemplar]

- (a) maximum when the battery is connected across  $1\text{cm} \times \frac{1}{2}\text{cm}$  faces.
- (b) maximum when the battery is connected across  $10\text{cm} \times 1\text{cm}$  faces.
- (c) maximum when the battery is connected across  $10\text{cm} \times \frac{1}{2}\text{cm}$  faces.
- (d) same irrespective of the three faces.

12. Which of the following characteristics of electrons determines the current in a conductor? [NCERT Exemplar]

- (a) Drift velocity alone
- (b) Thermal velocity alone
- (c) Both drift velocity and thermal velocity
- (d) Neither drift nor thermal velocity.

13. According to Joule's law, if potential difference across a conductor of material of resistivity remains constant, then heat produced in the conductor is directly proportional to

- (a)  $\frac{1}{\sqrt{\rho}}$
- (b)  $\rho$
- (c)  $\rho^{-1}$
- (d)  $\rho^2$

14. Two bulbs each marked 100 W, 220 V are connected in series across 220 V supply. The power consumed by them, when lit, is  
 (a) 220 W (b) 100 W (c) 50 W (d) zero

15. Two bulbs each marked 100 W, 220 V are connected in parallel across 220 V supply. The power consumed by them, when lit, is  
 (a) 200 W (b) 100 W (c) 50 W (d) zero

16. A 100 W, 200 V bulb is being operated at 160 V, the power dissipation is  
 (a) 32 W (b) 64 W (c) 100 W (d) 160 W


17. A 5°C rise in temperature is observed in a conductor by passing a current. If the current is doubled, the rise in temperature of the conductor will be nearly  
 (a) 10°C (b) 20°C (c) 40°C (d) 25°C

18. Temperature dependence of resistivity  $\rho(T)$  of semiconductors insulators and metals is significantly based on the following factors.  
 [NCERT Exemplar]

- (a) number of charge carriers can change with temperature  $T$ .
- (b) time interval between two successive collision can depend on  $T$ .
- (c) length of material can be a function of  $T$ .
- (d) mass of carriers is a function of  $T$ .

19. A wire of resistance  $12\Omega/m$  is bent to form a complete circle of radius 10 cm. The resistance between its two diametrically opposite points A and B as shown in figure is

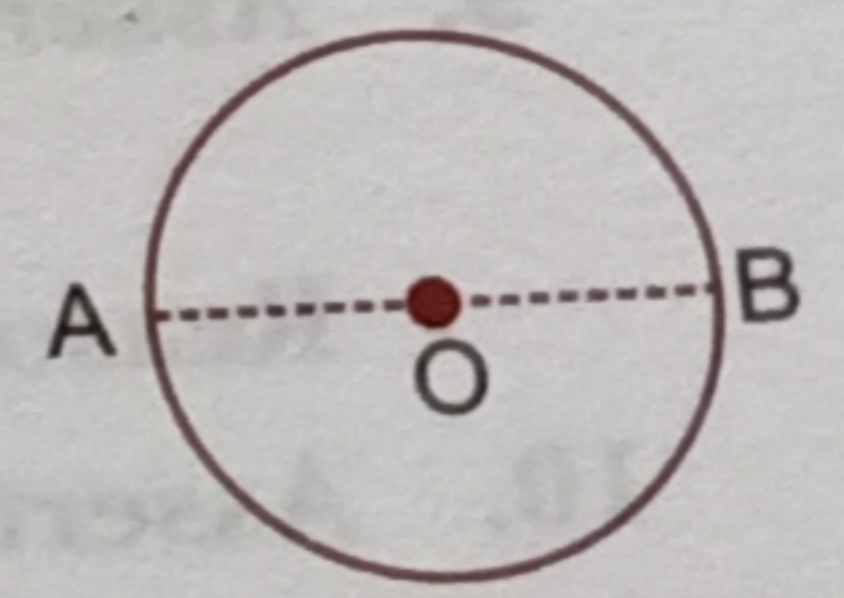- (a)  $3\Omega$
- (b)  $6\pi\Omega$
- (c)  $6\Omega$
- (d)  $0.6\pi\Omega$



[NCERT Exemplar]

20. Kirchhoff's junction rule is a reflection of

- (a) conservation of current density vector.
- (b) conservation of charge.
- (c) the fact that the momentum with which a charged particle approaches a junction is unchanged (as a vector) as the charged particle leaves the junction.
- (d) the fact that there is no accumulation of charged at a junction.